

Unit 1 MCQ Solutions

ECE-131

MCQ 1

The polarity of voltage drop across a resistor is determined by

- A. The value of the resistor
- B. The value of the current through resistor
- C. The direction of the current through resistor**
- D. The polarity of the source

MCQ 2

If 110 V is applied across 220 V, 100 W bulb, the power consumed by it will be

- A. 100 W
- B. 50 W
- C. 25 W**
- D. 12.5 W

MCQ 3

A resistance of 10 Ohm is connected across a supply of 200 V. When another resistance of R ohms is connected in parallel with the above 10 Ohm resistor, the current drawn from the supply doubles. The value of R is

- A. 5 Ohm
- B. 10 Ohm**
- C. 20 Ohm
- D. 22 Ohm

MCQ 4

The three resistance each of R ohms are connected in star. Its equivalent delta will comprise three resistance each of value

- A. $3R$**
- B. $2R$
- C. $R/2$
- D. $R/3$

MCQ 5

The three resistance each of R ohms are connected in delta. Its equivalent star will comprise three resistance each of value

- A. $3R$
- B. $2R$
- C. $R/2$
- D. $R/3$**

MCQ 6

Three resistors of 4 Ohm, 6 Ohm and 9 Ohm are connected in parallel in a network. Maximum power will be consumed by

- A. 4 Ohm**
- B. 6 Ohm
- C. 9 Ohm
- D. All of the resistors

MCQ 7


A current of 10 A enters a parallel combination of two resistance of 2 Ohm and 3 Ohm, Then the currents through these resistance will be

- A. 4 A, 6 A
- B. 6 A, 4 A**
- C. 2 A, 8 A
- D. 5 A, 5 A

MCQ 8

Find the equivalent resistance between points A and B in the network

- A. 3.4 Ohm
- B. 4 Ohm**
- C. 8 Ohm
- D. 40 Ohm

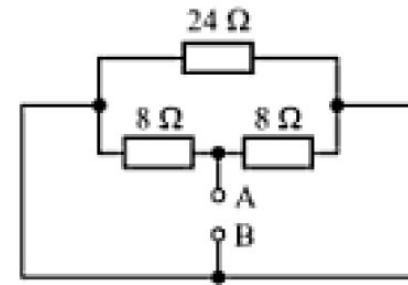

MCQ 9

Energy Stored in capacitor given by

A. C^2V

B. $C^2V/2$

C. $Q^2/2C$

D. CV

MCQ 10

If the voltage across the capacitor is increase by 2V, then the charge on the plates will

- A. Increase by 0.5 C
- B. Decrease by 0.5 C
- C. Decrease by 2 C
- D. Increase by 2 C**

MCQ 11


The number of equation required to analyze a given network by loop current method is equal to

- A. The number of independent loops
- B. The number of nodes
- C. The number of branches
- D. Number of nodes minus one (N-1)**

MCQ 12

Find the equivalent thevenin's resistance between terminals A and B in the circuit

- A. 6 V
- B. 6.25 V
- C. 6.5 V
- D. 6.75 V**

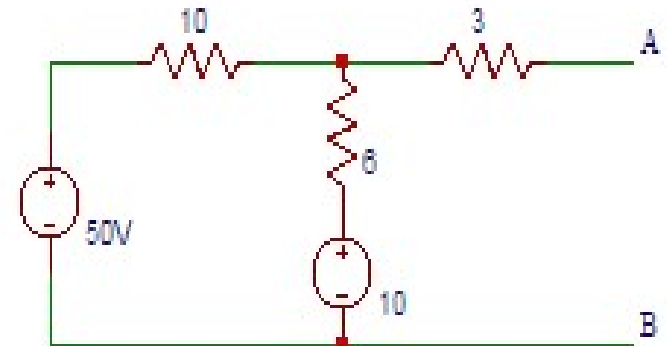

MCQ 13


Which of the following theorems is applicable for both linear and nonlinear circuits?

- A. Superposition
- B. Thevenin
- C. Norton
- D. None of these**

MCQ 14

Find the equivalent resistance between A and B.

- A. 32 Ohm
- B. 31 Ohm
- C. 30 Ohm
- D. 29 Ohm**

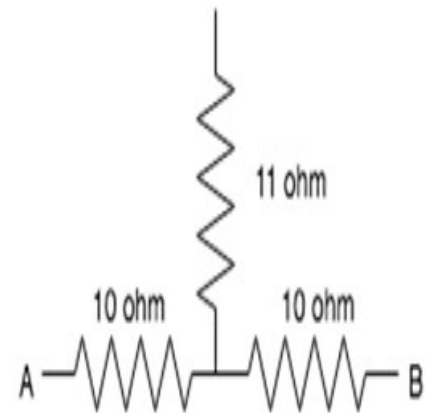

MCQ 15

Find the voltage across 2Ω resistor due to $20V$ source in the circuit shown below .

- A. 1.5 V**
- B. 1 V
- C. 2 V
- D. 2.5 V

