

UNIT-1

SEC: M1301

①

D.C. CIRCUITS

UID: 178911

VOLTAGE (or) POTENTIAL:-

→ The Amount of work done to bring a unit positive charge from  $\infty$  to a point is known as absolute potential of that point. We are interested in potential difference (Voltage) between two points.

→ If the Energy required to move a charge of  $Q$  coulombs from point A to point B is  $W$  Joules, the Voltage  $V$  between A and B is given as

$$V = \frac{W}{Q}$$

→ The unit of Voltage is Volt. 1 Volt = 1 Joule/coulomb

Energy:-

→ Capacity to do work is called as Energy. The unit of Energy is Joules.

→ If current is entering at the terminal of an element, then the element is absorbing the energy. Vice-versa.

POWER:-

→ Consider an element having a voltage  $V$  across it. A small charge  $\Delta q$  is moved through element from the positive terminal to the negative terminal in time  $\Delta t$ . The Energy  $\Delta W$  absorbed by the element in this process is given as  $\Delta W = V \Delta q$ .

$$\text{i.e. } \frac{\Delta W}{\Delta t} = V \cdot \frac{\Delta q}{\Delta t}$$

$$\Rightarrow \frac{dW}{dt} = \frac{dq}{dt} \cdot V = VI = P$$

→ The Rate of doing work is known as power.

$$P = VI$$

Generated by CamScanner from intsig.com

→ The unit of power is Watt (W).

Electromotive Force:-

→ It is the voltage of the Source when nothing is connected to it.

→ Electromotive force (EMF) is not a force. It is a voltage measured in Volts.

→ It is called force because it forces current to flow in a circuit.

Terminal Voltage:-

→ The voltage across the terminals of a Source is called its terminal voltage.

OHM'S LAW:-STATEMENT OF OHM'S LAW:-

It states that potential difference between two ends of a conductor is directly proportional to the current flowing through it, provided its temperature and other physical parameters remain unchanged. i.e.

$$V \propto I$$

$$\Rightarrow V = IR \text{ where } R \text{ is the constant of proportionality.}$$


→  $R$  is called Resistance and its unit is ohm ( $\Omega$ ).

Alternate way:-

$$I \propto V$$

$$\Rightarrow I = GV \text{ where } G \text{ is constant of proportionality}$$

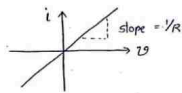→  $G$  is called Conductance of a conductor. It is a reciprocal of Resistance. SI unit of conductance is siemens (S).



OHM'S LAW in graphical form.

Applications of OHM'S LAW:-

- i)  $V=IR$ ,  $P=VI=I^2R = V^2/R$ . When two quantities are known, we can easily calculate the third quantity by using ohm's law.

Limitation of OHM'S LAW:-

1. This law can't be applied unilateral network. Eg: Network having Diodes etc.
2. ohm's law also not applicable for non-linear elements. Eg. Diode, Transistor etc.

POWER AND ENERGY IN RESISTOR:-

→ From ohm's law,  $V=IR$ .

$$\text{Power} = P = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = V \cdot I \text{ watt}$$

$$\Rightarrow \begin{aligned} P &= VI \text{ watt} \\ &= I^2 R \text{ watt} \\ &= V^2/R \text{ watt.} \end{aligned}$$

→ Energy (I will denote with E & W). is given by

$$P = \frac{dw}{dt} \text{ where } w \text{ is workdone (Energy).}$$

$$\Rightarrow P \cdot dt = dw$$

$$\Rightarrow \int P \cdot dt = \int dw.$$

$$\Rightarrow W \text{ \& } E = \int P \cdot dt \text{ J (or) Joule.}$$

$$\therefore E = \int VI \cdot dt = \int I^2 R \cdot dt = \int \frac{V^2}{R} \cdot dt.$$

Generated by CamScanner from intsig.com

POWER AND ENERGY IN CAPACITOR:-

→ The property of material which stores energy in an electric field is known as Capacitance. (C). units are Farad (F)

→ A Capacitance (C) satisfies a Relation,

$$i = C \cdot \frac{dv}{dt}$$

→ power in a Capacitor =  $p = V \cdot i$

$$\Rightarrow p = \frac{dv}{dt} \cdot C \cdot v$$

$$\Rightarrow p = C \cdot v \cdot \frac{dv}{dt} \text{ Watt.}$$

→ Energy in a Capacitor =  $E = \int P \cdot dt.$

$$= \int C \cdot v \cdot \frac{dv}{dt} \cdot dt$$

$$\Rightarrow E = \frac{1}{2} C v^2 \text{ Joule.}$$

POWER AND ENERGY IN INDUCTOR:-

→ The property of material which stores energy in magnetic field is known as Inductance. (L). units are Henry (H)

→ An Inductor satisfies a Relation,

$$V = L \cdot \frac{di}{dt}$$

→ power in an Inductor =  $p = Vi$

$$= L \cdot \frac{di}{dt} \cdot i$$

$$\Rightarrow p = L i \frac{di}{dt} \text{ Watt}$$

→ Energy in an Inductor =  $E = \int P \cdot dt = \int L i \frac{di}{dt} \cdot dt$

$$\Rightarrow E = \frac{1}{2} L i^2 \text{ Joule.}$$

Generated by CamScanner from intsig.com





SERIES AND PARALLEL COMBINATION OF R, L, C :-

→ When Three Resistances are in parallel. The Equivalent Resistance  $R_{eq}$  is given by.

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad \text{where } R_1, R_2 \text{ and } R_3 \text{ are given Resistances}$$

→ When  $R_1, R_2$  and  $R_3$  are in Series. Then  $R_{eq} = R_1 + R_2 + R_3$ .

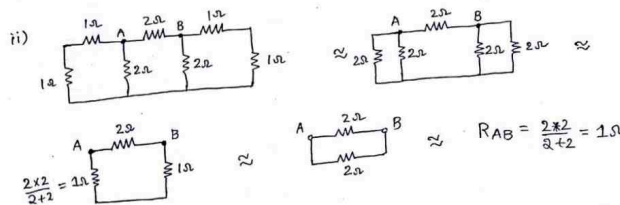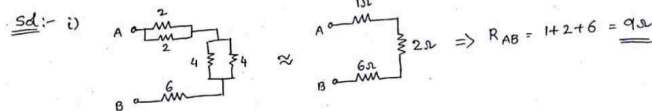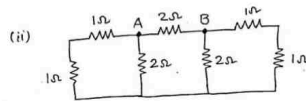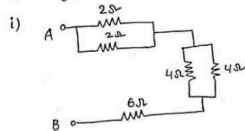⑦ Calculate Equivalent Resistance between A and B terminals in the following Circuits



→ When Three Inductances ( $L_1, L_2, L_3$ ) are in parallel, The Equivalent Inductance is given by.

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

→ When  $L_1, L_2, L_3$  are in Series.  $L_{eq} = L_1 + L_2 + L_3$  Henry.

Generated by CamScanner from intsig.com





→ When Three Capacitors are in parallel. The Equivalent Capacitance  $C_{eq}$  is given by

$$C_{eq} = C_1 + C_2 + C_3 \quad \text{where } C_1, C_2 \text{ and } C_3 \text{ are given capacitances}$$


→ When  $C_1, C_2$  and  $C_3$  are in Series. Then

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

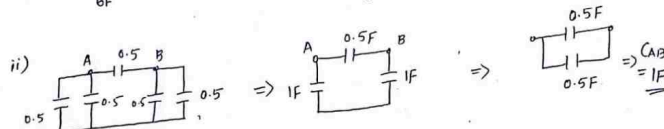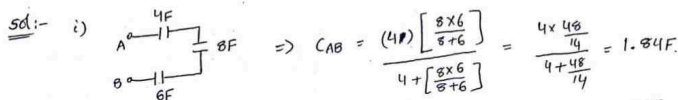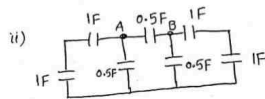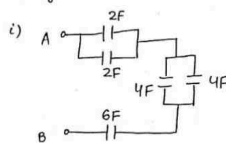⑧ Calculate Equivalent Capacitance between A and B terminals in the following Circuits.



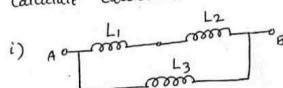⑨ Calculate Equivalent inductance b/w A and B terminals.



ii) If  $L_1 = 2H$ ,  $L_2 = 4H$ ,  $L_3 = 6H$ .  
 $L_{AB} = ?$

Sol:- i)


$$L_{AB} = \frac{L_3(L_1 + L_2)}{L_3 + L_1 + L_2}$$

ii)


$$L_{AB} = \frac{6(2 + 4)}{6 + 2 + 4} = 3H$$

Generated by CamScanner from intsig.com
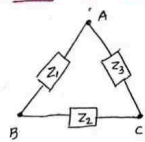
### STAR TO DELTA & DELTA TO STAR CONVERSION:-



Delta connection

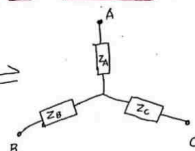

Star connection

→ Delta to Star Conversion:- (Assume above values of impedances)

$$Z_A = \frac{Z_1 Z_3}{Z_1 + Z_2 + Z_3}$$

$$Z_B = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3}$$

$$Z_C = \frac{Z_2 Z_3}{Z_1 + Z_2 + Z_3}$$

→ Star to Delta Conversion:-

$$Z_1 = Z_A + Z_B + \frac{Z_A Z_B}{Z_C}$$

$$Z_2 = Z_B + Z_C + \frac{Z_B Z_C}{Z_A}$$

$$Z_3 = Z_A + Z_C + \frac{Z_A Z_C}{Z_B}$$

→ In case Resistor,

i) Star to Delta:-

$$R_1 = R_A + R_B + \frac{R_A R_B}{R_C}$$

$$R_2 = R_B + R_C + \frac{R_B R_C}{R_A}$$

$$R_3 = R_A + R_C + \frac{R_A R_C}{R_B}$$

ii) Delta to Star:-

$$R_A = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

$$R_B = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_C = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

→ In case of Capacitor,

i) Star to Delta:-


$$\frac{1}{j\omega C_1} = \frac{1}{j\omega} \left[ \frac{1}{C_A} + \frac{1}{C_B} + \frac{C_C}{C_A C_B} \right]$$

$$\Rightarrow \frac{1}{C_1} = \frac{1}{C_A} + \frac{1}{C_B} + \frac{C_C}{C_A C_B}$$

Delta to Star

$$\frac{1}{C_A} = \frac{1/C_1 \cdot 1/C_3}{1/C_1 + 1/C_2 + 1/C_3}$$

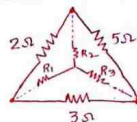④ If Delta connection is converted into star equivalent. Then calculate  $R_1, R_2, R_3$  values in the following network.




Sol:-

$$R_1 = \frac{2(3)}{2+3+5} = \frac{6}{10} = 0.6\Omega$$

$$R_2 = \frac{2(5)}{2+3+5} = \frac{10}{10} = 1\Omega$$




$$R_3 = \frac{3(5)}{2+3+5} = \frac{15}{10} = 1.5\Omega$$

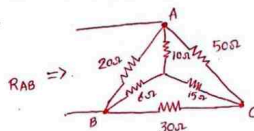⑤ Find Equivalent Resistance between A and B terminals in the following network.





Sol:-

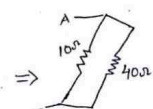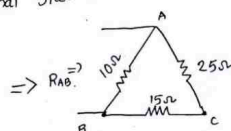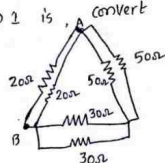Step 1 is convert internal star into Delta network.





$$\therefore R_{AB} = \frac{10(40)}{10+40} = \frac{400}{50} = 8\Omega$$

Hint:- convert

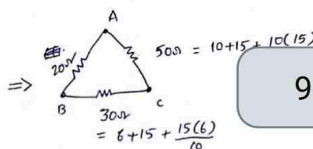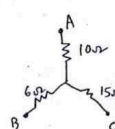

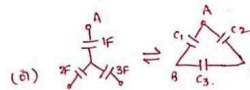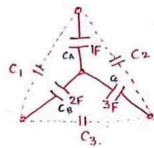Q. Convert the following network into its Delta equivalent form.



Calculate  $C_1, C_2$  and  $C_3$  if both are equivalent CKs.

Sol:-

$$\frac{1}{C_1} = \frac{1}{1} + \frac{1}{2} + \frac{1(1/2)}{1/3} = 1.5 + \frac{2}{3} = 3 \Rightarrow C_1 = \frac{1}{3} F$$


$$\text{mly } C_2 = \frac{C_A C_C}{C_A + C_B + C_C} = \frac{1(3)}{1+2+3} = \frac{3}{6} = \frac{1}{2} F.$$

You can obtain above formula after simplifying



$$\frac{1}{C_2} = \frac{1}{C_A} + \frac{1}{C_C} + \frac{C_B}{C_A C_C}$$

$$\Rightarrow C_2 = \frac{C_A C_C}{C_A + C_B + C_C}$$
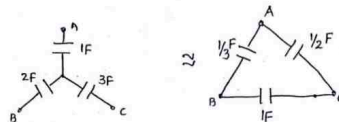
$$\text{mly } C_3 = \frac{C_B C_C}{C_A + C_B + C_C} = \frac{6}{1+2+3} = 1 F$$



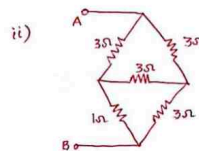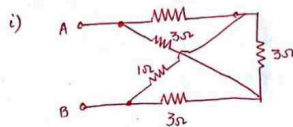Q. Calculate Equivalent Resistance between A and B terminals in the following Circuits.



Sol:-

i) and ii) Both are Same Circuits.




i) will be converted as (ii).

This is the first observation.

Generated by CamScanner from intsig.com

→ don't Apply wheatstone Bridge logic. It is not satisfying.  
i.e.  $3 \times 3 \neq 1 \times 3$ .

→ Convert  $\Delta$  network into star.

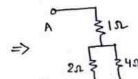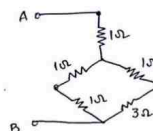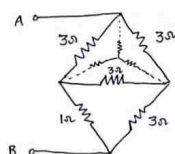

10

$$\Rightarrow R_{AB} = 1 + (2//4) = 1 + \frac{2(4)}{2+4} = \frac{7}{3} \Omega$$

→ H/W. Assume Capacitors and practice the above Model.

\* THE KIRCHHOFF'S LAWS:-

→ Kirchhoff's current Law (KCL)


→ Kirchhoff's Voltage Law (KVL)

1. KIRCHHOFF'S CURRENT LAW (KCL):-

In a Lumped electric Circuit, For any of its nodes, on that at any time 't', The Algebraic sum of branch currents leaving the node is Zero.

$$-i_1 - i_2 + i_3 + i_4 - i_5 - i_6 = 0.$$
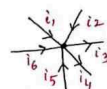
$$\Rightarrow i_1 + i_2 + i_5 + i_6 = i_3 + i_4$$




We can also define KCL as,  
Sum of entering Currents = Sum of leaving Currents at node.


→ KCL is independent of nature of elements connected to the Node.



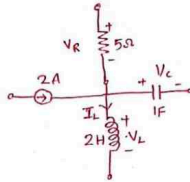- Q. If  $V_R = 5V$ ,  $V_C = 4\sin 2t$  then Calculate  $I_L$  and  $V_L$  in the following circuit.



Sol:- The given circuit is:

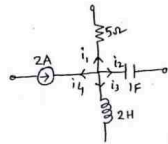

By KCL,  
 $i_1 + i_2 + i_3 + i_4 = 0$  ... (1)

$\Rightarrow i_1 = -\frac{V_R}{5\Omega} = \frac{5}{5} = -1$

$i_3 = I_L$

$i_2 = C \frac{dV_C}{dt} = 1 \cdot \frac{d}{dt} (4\sin 2t) = 8\cos 2t$


$i_3 = I_L = ?$

$i_4 = -2A$

$\therefore$  By KCL,  
 $-1 + 8\cos 2t + I_L - 2 = 0$   
 $\Rightarrow I_L = 3 - 8\cos 2t$  Amp.

$V_L = L \frac{dI_L}{dt} = 2 \cdot \frac{d}{dt} [3 - 8\cos 2t] = 32\sin 2t$  V

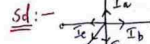- Q. Calculate  $i_2$  in following circuit



By KCL,  
 $i_1 + i_2 + i_3 + i_4 = 0$

$\Rightarrow -3 - i_2 - 6 - 5 - 4 = 0$


$\Rightarrow i_2 = -18$  A

Guru goud.

Generated by CamScanner from intsig.com

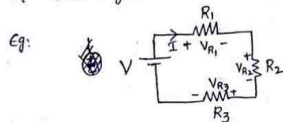
### KIRCHHOFF'S VOLTAGE LAW:-

In a Lumped electric circuit, for any of its loops and at any time 't', the Algebraic sum of branch voltages around (closed) loop is zero.




By KVL,  
 $-V + V_{R1} + V_{R2} + V_{R3} = 0$   
 $\Rightarrow V = V_{R1} + V_{R2} + V_{R3}$

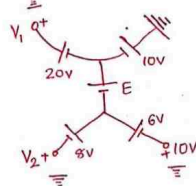- Q. Determine  $V_1$ ,  $V_2$ ,  $E$  for the following circuit.



12

Sol:-

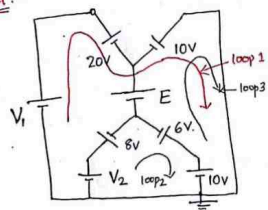

From loop 1,

$-V_1 + 20 - 10 = 0 \Rightarrow V_1 = 10V$

From loop 2,

$-V_2 + 8 - 6 + 10 = 0 \Rightarrow V_2 = 12V$

From loop 3,

$-10 + 6 - E - 10 = 0 \Rightarrow E = -14V$

### NODAL ANALYSIS & MESH ANALYSIS:-


KCL + OHM'S LAW  $\rightarrow$  NODAL ANALYSIS

KVL + OHM'S LAW  $\rightarrow$  MESH ANALYSIS.

$\rightarrow V = IR$  (OHM'S LAW). power in Resistor  $= I^2 R = \frac{V^2}{R} = V \cdot I$

Generated by CamScanner from intsig.com

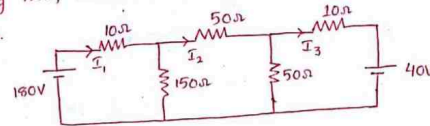
13) By using KVL, Calculate  $I_1, I_2, I_3$  currents in the following network.



After calculating  $I_1, I_2, I_3$ . Calculate

- power delivered by 180V Voltage Source
- power absorbed by 150Ω Resistor
- power absorbed by 40V voltage Source.
- Voltage across 150Ω resistor as well as 50Ω Resistor.

Sol:-

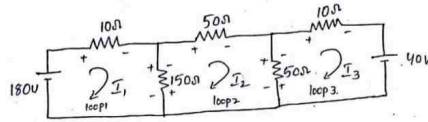

Apply KVL in loop 1,

$$-180 + 10(I_1) + 150(I_1 - I_2) = 0$$

$$\Rightarrow 160I_1 - 150I_2 = 180 \quad \text{--- (1)}$$

Apply KVL in loop 2,

$$50I_2 + 50(I_2 - I_3) + 150(I_2 - I_1) = 0$$

$$\Rightarrow -150I_1 + 250I_2 - 50I_3 = 0 \quad \text{--- (2)}$$

Apply KVL in loop 3,

$$10I_3 + 40 + 50(I_3 - I_2) = 0$$

$$\Rightarrow -50I_2 + 60I_3 = -40 \quad \text{--- (3)}$$

Solving (1), (2), (3) using Calculator,

$$I_1 = 3A$$

$$I_2 = 2A$$

$$I_3 = 1A$$

- power delivered by Voltage Source 180V =  $P = V(I_1) = 180(3) = 540 \text{ Watt}$

Generated by CamScanner from intsig.com

14) (ii) Current in 150Ω Resistor =  $I_{150\Omega} = I_1 - I_2 = 3 - 2 = 1A$ .

$$\therefore \text{power absorbed by } 150\Omega \text{ Resistor} = P_{150\Omega} = I_{150\Omega}^2 R = (1)^2 (150) = 150W$$


iii) power absorbed by 40V voltage Source.

$$P_{40} = V_4 I_3 = 40(1) = 40W$$

iv) Voltage across 150Ω =  $V_{150\Omega} = I_{150\Omega} (150\Omega) = 1(150) = 150V$


$$\text{Voltage across } 50\Omega = V_{50\Omega} = I_{50\Omega} (50\Omega) = I_2 (50) = 2(50) = 100V$$

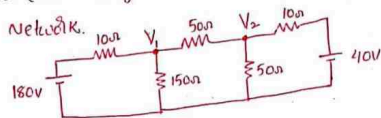15) By using KCL (Nodal Voltage Method), Calculate  $V_1$  and  $V_2$  in the following network.



Sol:-

The given circuit is,

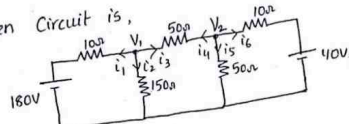

By applying KCL at node  $V_1$ ,

$$i_1 + i_2 + i_3 = 0$$

$$\Rightarrow \frac{V_1 - 180}{10} + \frac{V_1}{150} + \frac{V_1 - V_2}{50} = 0$$

$$\Rightarrow V_1 \left[ \frac{1}{10} + \frac{1}{150} + \frac{1}{50} \right] - \frac{V_2}{50} = 18$$

$$\Rightarrow \frac{19}{150} V_1 - \frac{V_2}{50} = 18 \quad \text{--- (1)}$$

By Applying KCL at node  $V_2$ ,

$$i_4 + i_5 + i_6 = 0$$

Generated by CamScanner from intsig.com

$$\frac{V_2 - V_1}{50} + \frac{V_2}{50} + \frac{V_2 - 40}{10} = 0.$$


$$\Rightarrow V_2 \left[ \frac{1}{50} + \frac{1}{50} + \frac{1}{10} \right] - \frac{V_1}{50} = 4$$

$$\Rightarrow \frac{7}{50} V_2 - \frac{1}{50} V_1 = 4. \quad \text{--- (2)} \quad \text{(or)} \quad -\frac{1}{50} V_1 + \frac{7}{50} V_2 = 4.$$


$$V_1 = 150V$$

$$V_2 = 50V.$$

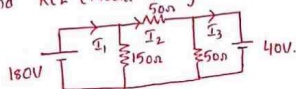Q. Calculate  $I_1$ ,  $I_2$  and  $I_3$  in the following circuit using KVL (Mesh Analysis) and KCL (Nodal Analysis).



Sol: i) KVL:

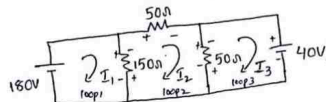

Apply KVL in loop 1,

$$-180 + 150(I_1 - I_2) = 0.$$

$$\Rightarrow 150I_1 - 150I_2 = 180 \quad \text{--- (1)}$$

Apply KVL in loop 2,

$$50I_2 + 50(I_2 - I_3) + 150(I_2 - I_1) = 0.$$

$$\Rightarrow -150I_1 + 250I_2 - 50I_3 = 0 \quad \text{--- (2)}$$

Apply KVL in loop 3,

$$50(I_3 - I_2) + 40 = 0.$$

$$\Rightarrow 50I_2 - 50I_3 = 40 \quad \text{--- (3)}$$

Solving (1), (2), (3)


$$I_1 = 4A$$

$$I_2 = 2.8A$$

$$I_3 = 2A$$

Generated by CamScanner from intsig.com

ii) KCL,

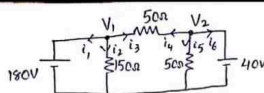

$$V_1 = 180V, \quad V_2 = 40V.$$

Apply KCL at node  $V_1$ ,

$$i_1 + i_2 + i_3 = 0.$$

$$\Rightarrow i_1 + \frac{V_1}{150} + \frac{V_1 - V_2}{50} = 0.$$

$$\Rightarrow i_1 = -\frac{V_1}{150} - \left( \frac{V_1 - V_2}{50} \right) = -\frac{180}{150} - \frac{140}{50} = -4A$$

$$\therefore I_1 = -i_1 = 4A$$

Apply KCL at node  $V_2$ ,

$$i_4 + i_5 + i_6 = 0.$$

$$\frac{V_2 - V_1}{50} + \frac{V_2}{50} + i_6 = 0.$$


$$\Rightarrow i_6 = \frac{V_1 - V_2}{50} - \frac{V_2}{50} = \frac{180 - 40}{50} - \frac{40}{50} = 2A$$

$$I_3 = i_6 = 2A.$$

$$I_2 = \frac{V_1 - V_2}{50} = \frac{180 - 40}{50} = \frac{140}{50} = 2.8A$$

16

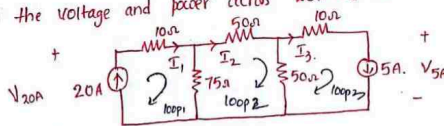Q. Calculate  $I_1$ ,  $I_2$ ,  $I_3$  in the following network. After calculation find the voltage and power across 20A and 5A current sources.




Sol: i) KVL, By looking at the circuit, we can easily say.

$$I_1 = 20A$$

$$I_3 = 5A.$$



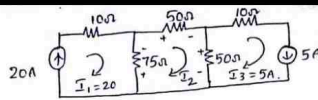

(17)

At loop2, By KVL,  $50I_2 + 75(I_2 - I_1) + 50(I_2 - I_3) = 0$ .


$$\Rightarrow 175I_2 = 75I_1 + 50I_3$$

$$= 75(20) + 50(5)$$

$$\Rightarrow I_2 = \frac{1500 + 250}{175} = 10A$$

$$\therefore \boxed{I_1 = 20A} \quad \boxed{I_2 = 10A} \quad \boxed{I_3 = 5A}$$

ii) By KCL,

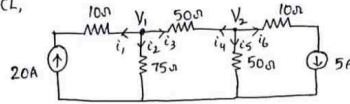

$$i_1 = -20A; \quad i_6 = 5A$$

Apply KCL at Node  $V_1$ ,

$$i_1 + i_2 + i_3 = 0$$

$$\Rightarrow -20 + \frac{V_1}{75} + \frac{V_1 - V_2}{50} = 0$$

$$\Rightarrow V_1 \left[ \frac{1}{75} + \frac{1}{50} \right] - \frac{V_2}{50} = 20 \quad \text{--- (1)}$$

Apply KCL at Node  $V_2$ ,

$$i_4 + i_5 + i_6 = 0$$

$$\frac{V_2 - V_1}{50} + \frac{V_2}{50} + 5 = 0$$

$$\Rightarrow -\frac{V_1}{50} + V_2 \left[ \frac{1}{50} + \frac{1}{50} \right] = -5 \quad \text{--- (2)}$$

Solving (1) & (2).

$$V_1 = 750V$$

$$V_2 = 250V$$

$$I_2 = \frac{V_1 - V_2}{50} = \frac{750 - 250}{50} = 10A$$


$$I_1 = -i_1 = 20A$$

$$I_3 = i_6 = 5A$$

Generated by CamScanner from intsig.com

we have to calculate voltage and power across Current Sources.

(18)

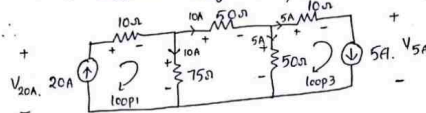

→ In loop1, Apply KVL,  $-V_{20A} + 10(20) + 75(10) = 0$ .

$$\Rightarrow V_{20A} = 950V$$

i.e. voltage across Current source  $20A = 950V$ .

$$\therefore \text{power delivered by } 20A \text{ Current Source} = P_{20} = V_{20A} \cdot I_{20A}$$

$$= 950(20) = 19 \text{ Kwatt}$$

→ In loop3, Apply KVL,


$$+V_{5A} - 50(5) + 5(10) = 0$$

$$\Rightarrow V_{5A} = 250 - 50 = 200V$$


$$\therefore \text{power absorbed by } 5A \text{ current Source} = P_5 = V_{5A} (I_{5A}) = 200(5)$$

$$= 1 \text{ kW}$$

Note:-

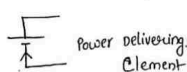


Power delivering element

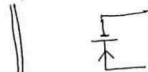

Power absorbing element

Q. H/w.

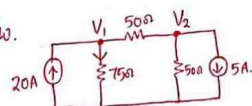


Calculate  $V_1$  and  $V_2$  and current across  $75\Omega$  Resistor.

$$\text{Ans: } V_1 = 750V$$

18


Q. H/w.

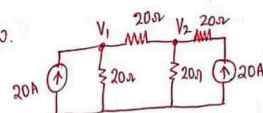


Calculate  $V_1$  and  $V_2$ .

Hint: Apply Above procedure. you will get Answer.

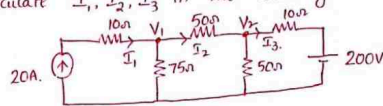Q. Calculate  $I_1, I_2, I_3$  in the following circuit. (Use KCL).



Sol:- The given circuit is

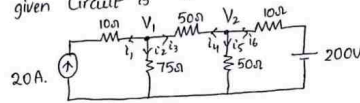

$$i_1 = -20A$$

$$\Rightarrow I_1 = -i_1 = 20A$$

Apply KCL at Node  $V_1$ ,

$$i_1 + i_2 + i_3 = 0$$

$$\Rightarrow -20 + \frac{V_1}{75} + \frac{V_1 - V_2}{50} = 0$$

$$\Rightarrow V_1 \left[ \frac{1}{75} + \frac{1}{50} \right] - \frac{V_2}{50} = 20$$

$$\text{--- (1)}$$

Apply KCL at Node  $V_2$ ,

$$i_4 + i_5 + i_6 = 0$$

$$\frac{V_2 - V_1}{50} + \frac{V_2}{50} + \frac{V_2 - 200}{10} = 0$$

$$\Rightarrow -\frac{V_1}{50} + V_2 \left[ \frac{1}{50} + \frac{1}{50} + \frac{1}{10} \right] = 20$$

$$\text{--- (2)}$$

Solving (1) and (2).

$$V_1 = 750V$$

$$V_2 = 250V$$

$$\therefore I_2 = \frac{V_1 - V_2}{50} = \frac{750 - 250}{50} = 10A$$



$$I_3 = \frac{V_2 - 200}{10} = \frac{50}{10} = 10A$$

$$I_1 = -i_1 = 20A$$

→ This completes KVL and KCL topic. (Exam point of view only)

→ practice problems Based on wheat stone Bridge + KVL + KCL type.

Eg:-

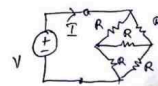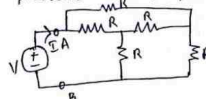


Calculate  $I$

Generated by CamScanner from intsig.com

Q. Determine the unknown Resistance 'R'. (KVL & KCL).


H/W.

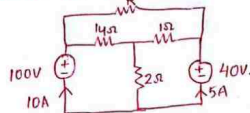



$$\text{Ans: } R = 12\Omega$$

Q. Determine potential between p and q in following circuit.

$$\text{Ans: } V_{pq} = -6V$$

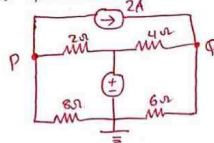


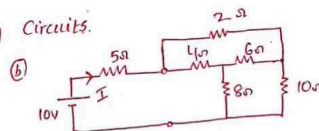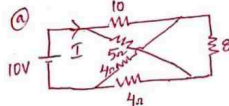Q. Calculate  $I$  for the following circuits.



Hint: Above two are of Bridge circuit

→ VOLTAGE DIVISION :-

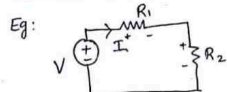

Apply KVL,

$$-V + IR_1 + IR_2 = 0$$


$$\Rightarrow V = IR_1 + IR_2$$

$$\Rightarrow I = \frac{V}{R_1 + R_2}$$

$$V_{R_1} = IR_1 = \frac{I \cdot R_1}{R_1 + R_2}$$

$$V_{R_2} = I \cdot R_2 = \frac{I \cdot R_2}{R_1 + R_2}$$

→ CURRENT DIVISION

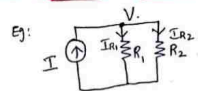

By KCL,  $I = I_{R_1} + I_{R_2}$

$$\Rightarrow I = \frac{V}{R_1} + \frac{V}{R_2}$$

$$\Rightarrow V = \frac{I}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$\therefore I_{R_1} = \frac{V}{R_1} = \frac{I}{\left(\frac{1}{R_1} + \frac{1}{R_2}\right) R_1} = \frac{I \cdot R_2}{(R_1 + R_2) R_1} = \frac{I \cdot R_2}{R_1 + R_2}$$


$$\text{Similarly } I_{R_2} = I \cdot \frac{R_1}{R_1 + R_2}$$

Generated by CamScanner from intsig.com





## → SOURCE TRANSFORMATION :-

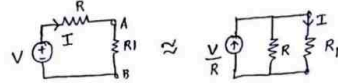(21)

→ we can Represent Voltage Source in Series with Resistance as Current Source with parallel Resistance. Vice-versa.



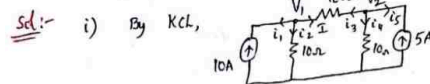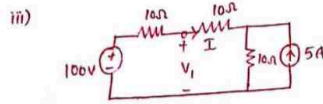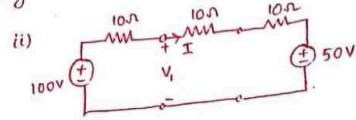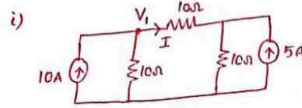Q. Calculate  $V_1$  and  $I$  in the following Circuits.



At  $V_1$ ,  $i_1 + i_2 + I = 0$ .

$\Rightarrow -10 + \frac{V_1}{10} + \frac{V_1 - V_2}{10} = 0$ .

$\Rightarrow 2V_1 - V_2 = 100$  — (1).

At  $V_2$ ,  $i_3 + i_4 + i_5 = 0$ .


$\Rightarrow \frac{V_2 - V_1}{10} + \frac{V_2}{10} - 5 = 0$ .  $\Rightarrow V_1 - 2V_2 = -50$  — (2).

Solving (1) & (2).  $V_1 = \frac{250}{3}V$ .  $V_2 = \frac{200}{3}V$ .

$V_1 = \frac{250}{3}V$ ,  $I = 1.67A$

$\therefore I = \frac{V_1 - V_2}{10} = \frac{250 - 200}{3(10)} = 1.67A$

ii) By KVL,

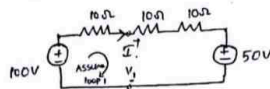

$-100 + 30(I) + 50 = 0$ .

$\Rightarrow I = \frac{50}{30} = 1.67A$ .

$-100 + 10(1.67) + V_1 = 0$ .  $\Rightarrow V_1 = 83.3V \approx \frac{250}{3}V$ .


$V_1 = \frac{100 - 10I}{1} = \frac{250}{3}V$ .

Generated by CamScanner from intsig.com


iii) H/w.  $V_1 = \frac{250}{3}V$ ,  $I = 1.67A$  (check it)

(22)


## → IDEAL VOLTAGE SOURCE

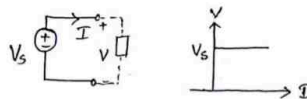


## PRACTICAL VOLTAGE SOURCE

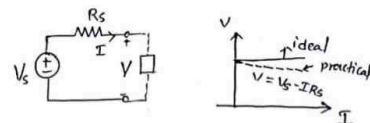

## → IDEAL CURRENT SOURCE

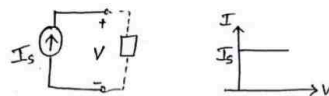

## PRACTICAL CURRENT SOURCE

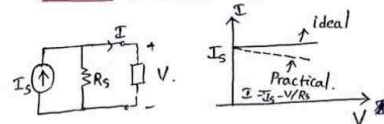

## → DEPENDENT SOURCES :-

→ VCVC

→ VCCS

→ CCVS

→ CCCS

} Not in Syllabus. Basics is Sufficient  
Problems Not Required. - GROUND.